

Record good times

DIODE FUNDAMENTALS

SAMPLE PROBLEM: FOR DIODE CURVE IN FIG. 5, CALCULATE THE DC RESISTANCE, R_F @ POINTS A & B.

Sol'n:

$$\text{POINT A: } R_F = \frac{V_F}{I_F} = \frac{0.65V}{11mA} = 59.1 \Omega //$$

$$\text{POINT B: } R_F = \frac{V_F}{I_F} = \frac{0.7V}{22.5mA} = 31.1 \Omega //$$

* CONVERT mA to A

SAMPLE PROBLEM: DETERMINE THE DC RESISTANCE LEVELS FOR THE DIODE OF THE FIGURE SHOWN IF (a) $I_F = 2mA$, (b) $I_F = 20mA$ and (c) $V_F = -10V$

Sol'n: (a) $I_F = 2mA$

$$R_F = \frac{V_F}{I_F} = \frac{0.5V}{2mA} = \frac{0.5V}{0.002A}$$

$$R_F = 250 \Omega //$$

(b) $I_F = 20mA$

$$R_F = \frac{V_F}{I_F} = \frac{0.8V}{0.020A}$$

$$R_F = 40 \Omega //$$

(c) $V_F = -10V$

$$R_F = \frac{V_F}{I_F} = \frac{-10V}{0A}$$

$$= \text{infinite}$$

resistance
The I_F is zero, this means the diode is not conducting. In this case, the resistance would be extremely high (infinite)

SAMPLE PROBLEM: A SILICON DIODE HAS FORWARD VOLTAGE DROP OF 1.1V DIODE CURRENT, I_F , OF 1A. CALCULATE THE BULK RESISTANCE, R_B

Sol'n:

$$R_B = \frac{\Delta V}{\Delta I}$$

$$= \frac{1.1V - 0.7V}{1A - 0A}$$

$$= \frac{0.4V}{1A}$$

$$= 0.4 \Omega //$$

* 0.7V is the required voltage for silicon diode to enable current to begin flowing through the diode.

Record good times

SAMPLE PROBLEM: WITH FIGURE SHOWN BELOW, SOLVE FOR THE LOAD VOLTAGE AND CURRENT USING FIRST, AND SECOND, AND THIRD APPROXIMATION.

Sol'n:

• FIRST APPROXIMATION: SEE FIG (b)

$$V_L = V_{IN} = 10V_{dc}$$

$$I_L = \frac{V_L}{R_L} = \frac{10V}{100\Omega} = \text{100mA or } 100\text{mA}$$

• SECOND APPROXIMATION: SEE FIG (c)

$$\begin{aligned} V_L &= V_{IN} - V_B \\ &= 10V - 0.7V \\ &= 9.3V \end{aligned}$$

$$I_L = \frac{V_L}{R_L} = \frac{9.3V}{100\Omega} = 0.093A \text{ or } 93\text{mA}$$

• THIRD APPROXIMATION SEE FIG (d)

$$\begin{aligned} I_L &= \frac{V_{IN} - V_B}{R_L + r_B} \\ &= \frac{10V - 0.7V}{100\Omega + 2.5\Omega} \\ &= \frac{9.3V}{102.5\Omega} \end{aligned}$$

$$\begin{aligned} V_L &= I_L R_L \\ &= (90.73\text{mA})(100\Omega) \\ &= (0.0907A)(100\Omega) \end{aligned}$$

$$V_L = 9.07V$$

$$= 0.0907A$$

$$\text{or } 90.73\text{mA}$$

SPECIAL DIODES: LIGHT EMITTING DIODES

SAMPLE PROBLEM: CALCULATE THE LED CURRENT IN FIGURE 10a.

Sol'n: THE CURRENT THROUGH LED CAN BE FOUND BY DIVIDING THE RESISTOR VOLTAGE BY ITS RESISTANCE. ASSUME THE LED HAS A VOLTAGE DROP OF 2.0V.

$$I_{LED} = \frac{V_{IN} - V_{LED}}{R_S}$$

$$= \frac{24V - 2V}{2.2k\Omega} = \frac{22V}{2,200\Omega}$$

$$= 0.01A \text{ or } 10\text{mA}$$

Record good times

SAMPLE PROBLEM: IN FIGURE 10b, calculate the resistance, R_S , required to provide an LED current, 25mA.

Sol'n: As stated previously, assume a forward voltage of 2.0V for an LED.

$$R_S = \frac{V_{IN} - V_{LED}}{I_{LED}} = \frac{24V - 2V}{25mA}$$
$$= \frac{22V}{0.025A}$$

$$R_S = 880 \Omega //$$

SPECIAL DIODES: ZENER DIODES

SAMPLE PROBLEM: CALCULATE THE MAXIMUM-RATED ZENER CURRENT FOR A 1-W, 10V ZENER.

Sol'n:

$$I_{Zm} = \frac{P_{Zm}}{V_Z}$$
$$= \frac{1W}{10V}$$

$$= 0.1A \text{ or } 100mA //$$

SAMPLE PROBLEM: IF $V_Z = 10V$ IN FIG. 12, CALCULATE I_Z .

$$I_Z = \frac{V_{IN} - V_Z}{R_S} = \frac{25V - 10V}{1k\Omega} = \frac{15V}{1000\Omega} = 0.015A \text{ or } 15mA$$

SAMPLE PROBLEM: IF R_L INCREASES TO 250Ω IN FIG. 13, CALCULATE THE FF. I_S , I_L , I_Z , and P_Z

• I_S remains constant at 75mA even through R_L change because V_{IN} , V_Z and R_S remaining constant.

$$• I_L = \frac{V_Z}{R_L} = \frac{7.5V}{250\Omega} = 0.03A \text{ or } 30mA //$$

$$• I_Z = I_S - I_L$$
$$= 75mA - 30mA$$
$$= 45mA //$$

$$• P_Z = V_Z I_Z$$
$$= (7.5V)(45mA)$$
$$= 337.5mW //$$

Record good times

PROPER TRANSISTOR BIASING

SAMPLE PROBLEM: A TRANSISTOR HAS THE FF. CURRENTS $I_B = 20 \text{ mA}$ and $I_C = 4.98 \text{ A}$, CALCULATE I_E ,

Sol'n:
$$I_E = I_B + I_C$$
$$= 20 \text{ mA} + 4.98 \text{ A}$$
$$= 0.02 \text{ A} + 4.98 \text{ A}$$
$$I_E = 5 \text{ A} //$$

SAMPLE PROBLEM: A TRANSISTOR HAS THE FF. CURRENTS $I_E = 100 \text{ mA}$ and $I_B = 1.96 \text{ mA}$, CALCULATE I_C

Sol'n:
$$I_C = I_E - I_B$$
$$= 100 \text{ mA} - 1.96 \text{ mA}$$
$$I_C = 98.04 \text{ mA} //$$

SAMPLE PROBLEM: A TRANSISTOR HAS THE FF. CURRENTS $I_E = 50 \text{ mA}$ AND $I_C = 49 \text{ mA}$, CALCULATE I_B .

Sol'n:
$$I_B = I_E - I_C$$
$$= 50 \text{ mA} - 49 \text{ mA}$$
$$I_B = 1 \text{ mA} //$$

SAMPLE PROBLEM: A TRANSISTOR HAS THE FF. $I_E = 15 \text{ mA}$, $I_B = 60 \mu\text{A}$, CALCULATE α_{dc} ,

Sol'n:
$$I_C = I_E - I_B$$
$$= 15 \text{ mA} - 60 \mu\text{A}$$
$$= 15 \text{ mA} - 0.06 \text{ mA}$$
$$I_C = 14.94 \text{ mA} //$$

$$\alpha_{dc} = \frac{I_C}{I_E}$$
$$= \frac{14.94 \text{ mA}}{15 \text{ mA}}$$

$$\alpha_{dc} = 0.996 //$$

Record good times

SAMPLE PROBLEM: A TRANSISTOR HAS THE β_{dc} CURRENT $I_C = 10 \text{ mA}$, $I_B = 50 \mu\text{A}$, CALCULATE β_{dc} .

Sol'n:
$$\beta_{dc} = \frac{I_C}{I_B} = \frac{10 \text{ mA}}{50 \mu\text{A}} = \frac{10 \text{ mA}}{0.05 \text{ mA}} = 200$$

SAMPLE PROBLEM: A TRANSISTOR HAS $\beta_{dc} = 150$ and $I_B = 75 \mu\text{A}$, CALCULATE I_C .

Sol'n:
$$\beta_{dc} = \frac{I_C}{I_B}$$

$$\begin{aligned} I_C &= \beta_{dc} I_B \\ &= (150)(75 \mu\text{A}) \\ &= (150)(0.075 \text{ mA}) \end{aligned}$$

$$I_C = 11.25 \text{ mA}$$

SAMPLE PROBLEM: A TRANSISTOR HAS $\beta_{dc} = 100$ CALCULATE α_{dc} .

$$\alpha_{dc} = \frac{\beta_{dc}}{1 + \beta_{dc}} = \frac{100}{1 + 100} = 0.99$$

SAMPLE PROBLEM: A TRANSISTOR HAS $\alpha_{dc} = 0.995$, CALCULATE β_{dc}

$$\beta_{dc} = \frac{\alpha_{dc}}{1 - \alpha_{dc}} = \frac{0.995}{1 - 0.995} = 199$$

SAMPLE PROBLEM: IN THE FIGURE SHOWN BELOW, SOLVE FOR I_B , I_C , and V_{ce} .

Sol'n:

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$= \frac{5 \text{ V} - 0.7 \text{ V}}{56 \text{ k}\Omega} \quad \text{* since the transistor is silicon, } V_{BE} = 0.7 \text{ V}$$

$$= \frac{4.3 \text{ V}}{56,000 \Omega}$$

$$= 7.68 \mu\text{A}$$

Record good times

$$I_c = \beta_{dc} I_B$$

$$= (100)(76.78 \mu A)$$

$$I_c = 7.68 \text{ mA} //$$

$$V_{CE} = V_{CC} - I_c R_c$$

$$= 15 \text{ V} - (7.68 \text{ mA} \times 1 \text{ k}\Omega)$$

$$= 15 \text{ V} - 7.68 \text{ V}$$

$$V_{CE} = 7.32 \text{ V} //$$

SAMPLE PROBLEM: IN FIGURE SHOWN BELOW, SOLVE FOR I_B , I_c , and V_{CE}

SOLN:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{15 \text{ V} - 0.7 \text{ V}}{180 \text{ k}\Omega} = \frac{14.3 \text{ V}}{180 \text{ k}\Omega} = 79.44 \mu A$$

$$I_c = \beta_{dc} I_B$$

$$= (100)(79.44 \mu A)$$

$$= 7.94 \text{ mA}$$

$$V_{CE} = V_{CC} - I_c R_c$$

$$= 15 \text{ V} - (7.94 \text{ mA} \times 1 \text{ k}\Omega)$$

$$= 15 \text{ V} - 7.94 \text{ V}$$

$$V_{CE} = 7.06 \text{ V}$$

SAMPLE PROBLEM: IN FIGURE SHOWN BELOW, SOLVE FOR I_B , I_c , & V_{CE} .

SOL'n:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{390 \text{ k}\Omega} = 28.97 \mu A //$$

$$I_c = \beta_{dc} I_B$$

$$= (150)(28.97 \mu A)$$

$$I_c = 4.35 \text{ mA} //$$

$$V_{CE} = V_{CC} - I_c R_c$$

$$= 12 \text{ V} - (4.35 \text{ mA} \times 1.5 \text{ k}\Omega)$$

$$= 12 \text{ V} - 6.52 \text{ V}$$

$$V_{CE} = 5.48 \text{ V} //$$

Record good times

SAMPLE PROBLEM: FOR THE CIRCUIT SHOWN IN THE FIGURE BELOW, SOLVE FOR V_B , V_E , I_E , V_C and V_{CE}

Sol'n:

$$\begin{aligned} \bullet V_E &= V_B - V_{BE} \\ &= 2.38V - 0.7V \\ &= 1.68V \end{aligned}$$

$$I_E = \frac{V_E}{R_E} = \frac{1.68V}{240\Omega} = 7mA$$

$$\bullet I_E \approx I_C = 7mA$$

$$\begin{aligned} \bullet V_C &= V_{CC} - I_C R_C \\ &= 15V - (7mA \times 1k\Omega) \\ &= 15V - 7V \end{aligned}$$

$$V_C = 8V$$

$$\begin{aligned} \bullet V_{CE} &= V_{CC} - I_C (R_C + R_E) \\ &= 15V - 7mA (1k\Omega + 240\Omega) \\ &= 15V - 7mA (1000\Omega + 240\Omega) \\ &= 15V - 7mA (1240\Omega) \\ &= 15V - 0.007A (1240\Omega) \\ &= 15V - 8.68V \end{aligned}$$

$$V_{CE} = 6.32V$$

SAMPLE PROBLEM: FOR CIRCUIT SHOWN IN THE FIG. BELOW, SOLVE FOR V_B , V_E , I_C , V_C and V_{CE} .

Sol'n: $\bullet V_B = \frac{R_2}{R_1 + R_2} \times V_{CC}$

$$= \frac{5.6k\Omega}{53k\Omega + 5.6k\Omega} \times 18V = \frac{5.6k\Omega}{58.6k\Omega} \times 18V$$

$$= (0.1451k\Omega)(18V)$$

$$V_B = 2.61V$$

$$\begin{aligned} \bullet V_E &= V_B - V_{BE} \\ &= 2.61V - 0.7V \end{aligned}$$

$$V_E = 1.91V$$

$$\begin{aligned} \bullet I_E &= \frac{V_E}{R_E} = \frac{1.91V}{390\Omega} \\ &= 4.9mA \end{aligned}$$

$$\begin{aligned} \bullet V_C &= V_{CC} - I_C R_C \\ &= 18V - (4.9mA \times 1.5k\Omega) \end{aligned}$$

$$= 18V - 7.35V$$

$$V_C = 10.65V$$

$$\bullet V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$= 18V - 4.9mA (1.5k\Omega + 390\Omega)$$

$$= 18V - 4.9mA (1890\Omega)$$

$$= 18V - 9.261V$$

$$= 8.74V$$

SINCE $\beta_{DC} = 200$, $I_C \approx I_E = 4.9mA$

Record good times

SAMPLE PROBLEM: FOR THE PNP TRANSISTOR IN THE FIGURE BELOW, SOLVE FOR V_B , V_E , I_C , V_C & V_{CE}

SOL'N:

$$\begin{aligned} \bullet V_B &= \frac{R_2}{R_1 + R_2} (-V_{CC}) \\ &= \frac{6.2k\Omega}{6.2k\Omega + 33k\Omega} (-12V) \\ &= \frac{6.2k\Omega}{39.2k\Omega} (-12V) \\ &= (0.1581k\Omega)(-12V) \end{aligned}$$

$$V_B = -1.90V //$$

$$\begin{aligned} \bullet V_E &= V_B - V_{BE} \\ &= -1.9V - (-0.7V) \end{aligned}$$

$$V_E = -1.2V //$$

$$\bullet \text{ Since } I_E \approx I_C$$

$$I_C = \frac{V_E}{R_E} = \frac{1.2V}{500\Omega} = 2.4mA //$$

$$\begin{aligned} \bullet V_C &= -V_{CC} + I_C R_C \\ &= -12V + (2.4mA \times 2k\Omega) \\ &= -12V + (0.0024A \times 2000\Omega) \\ &= -12V + 4.8V \end{aligned}$$

$$V_C = -7.2V //$$

$$\begin{aligned} \bullet V_{CE} &= -V_{CC} + I_C (R_C + R_E) \\ &= -12V + 2.4mA (2k\Omega + 500\Omega) \\ &= -12V + 0.0024A (2000\Omega + 500\Omega) \\ &= -12V + 0.0024A (2500\Omega) \\ &= -12V + 6 \end{aligned}$$

$$V_{CE} = -6V //$$

SAMPLE PROBLEM: IN FIG. SHOWN BELOW, CALCULATE I_E & V_C

$$\begin{aligned} \text{SOL'N: } I_E &= \frac{V_{BE} - V_{RE}}{R_E} \\ &= \frac{6V - 0.7V}{1k\Omega} \\ &= \frac{5.3V}{1000\Omega} \end{aligned}$$

$$I_E = 0.0053A$$

$$\text{OR } 5.3mA //$$

$$\begin{aligned} V_C &= V_{CC} - I_C R_C \\ &= 15V - (5.3mA \times 1.5k\Omega) \\ &= 15V - (0.0053A \times 1500\Omega) \\ &= 15V - 7.95V \end{aligned}$$

$$V_C = 7.05V //$$

Record good times

SAMPLE PROBLEM: IN THE FIGURE SHOWN BELOW, CALCULATE I_E AND V_C

SOLN: • $I_E = \frac{V_{EF} - V_{BE}}{R_E} = \frac{10V - 0.7V}{2.2k\Omega} = \frac{9.3V}{2200\Omega}$

$$I_E = 0.00423A \text{ or } 4.23mA$$

ALTERNATIVE SOLUTION FOR I_E

$$I_E = \frac{V_{EF} - V_{BE}}{R_E + \frac{R_B}{\beta_{AC}}} = \frac{10V - 0.7V}{2.2k\Omega + \frac{1k\Omega}{200}} = \frac{9.3V}{2200\Omega + \frac{1000\Omega}{200}}$$

$$I_E = \frac{9.3V}{2200\Omega + 5\Omega} = \frac{9.3V}{2205\Omega} = 0.00421A \text{ or } 4.21mA$$

• $V_C = V_{CC} - I_C R_C$
 $= 10V - (4.23mA \times 1k\Omega)$
 $= 10V - (0.00423A \times 1000\Omega)$
 $= 10V - 4.23V$

$$V_C = 5.77V$$